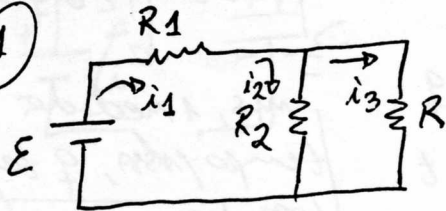


CAPÍTULO 10.

1



$$R_1 = 20\Omega$$

$$R_2 = 60\Omega$$

$$i_1 = i_2 + i_3$$

$$i_2 = i_1 - i_3$$

$$\begin{cases} E - 20i_1 - 60i_2 = 0 \\ -60i_2 + Ri_3 = 0 \end{cases}$$

$$i_2 = \frac{Ri_3}{60}$$

$$E - 20(i_2 + i_3) - 60i_2 = 0$$

$$E - 80i_2 - 20i_3 = 0$$

$$E - \frac{80Ri_3}{60} - 20i_3 = 0$$

$$E - \frac{4}{3}Ri_3 - 20i_3 = 0$$

$$i_3 = \left(20 + \frac{4}{3}R\right) = E$$

$$i_3 = \frac{E}{\left(20 + \frac{4}{3}R\right)}$$

A potência dissipada no resistor será:


$$P_R = Ri_3^2 = \frac{RE^2}{\left(20 + \frac{4}{3}R\right)^2}$$

$$\frac{dP_R}{dR} = \frac{-\left(20 + \frac{4}{3}R\right)^2 \cdot E^2 - RE^2 \left[2\left(20 + \frac{4}{3}R\right) \cdot \frac{4}{3}\right]}{\left(20 + \frac{4}{3}R\right)^4} = 0$$

$$\frac{dP_R}{dR} = \left(20 + \frac{4}{3}R\right)^{-2} E^2 = R E^2 \frac{8}{3} \left(20 + \frac{4}{3}R\right)^{-3}$$

$$20 + \frac{4}{3}R = \frac{8}{3}R$$
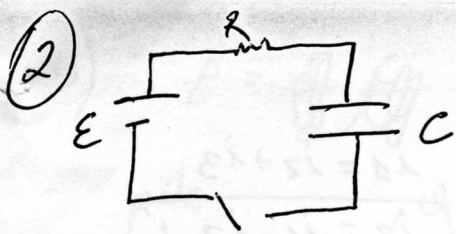
$$20 = \frac{4}{3}R \Rightarrow R = \frac{60}{4} \Rightarrow \boxed{R = 15\Omega}$$



$$E - Ri - \frac{q}{C} = 0$$

$$\begin{cases} dE_b = Edq \\ dE_R = Ri^2 dt \end{cases}$$

$$E_b = \int_0^q Edq = E \cdot q$$

mas, a medida que o tempo passa, q tende a E

Logo, $E_b = E \cdot EC = CE^2$


que é a energia produzida pela bateria.

$$C = \frac{q}{V}; \quad i(t) = i_0 e^{-t/\tau}; \quad \tau = RC; \quad E = Ri$$

$$E_R = \int dE_R = \int_0^{\infty} Ri^2 dt = R \int_0^{\infty} \left(\frac{E}{R}\right)^2 e^{-2t/\tau} dt$$

$$\frac{E^2}{R} \int_0^{\infty} e^{-2t/\tau} dt = \frac{E^2}{R} \left[\frac{-\tau}{2} \cdot e^{-2t/\tau} \right]_0^{\infty} \quad e^{-2t/\tau} \Big|_0^{\infty} = \frac{1}{e^{\infty}} - \frac{1}{e^0} (0-1)$$
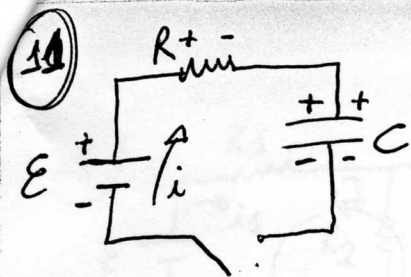
$$\frac{E^2}{R} \frac{\tau}{(-2)} (0-1) = \frac{E^2}{R} \frac{\tau}{2} = \boxed{\frac{E^2 C}{2}}$$



$$a) \quad V_E + V_R + V_C = 0 \quad \left\{ \begin{array}{l} V_E = +E \\ V_R = -R \cdot I \\ V_C = -\frac{Q}{C} \end{array} \right.$$

$$E - R \cdot I - \frac{Q}{C} = 0 \quad \therefore I = \frac{dQ}{dt}$$

$$-R \frac{dQ}{dt} - \frac{Q}{C} = -E \Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = E \quad \div (R)$$

$$\boxed{\frac{dQ}{dt} + \frac{Q}{RC} = \frac{E}{R}}$$

$$+ E - R \cdot I - \frac{Q}{C} = 0$$

$$0 - R \frac{dI}{dt} - \frac{1}{C} \frac{dQ}{dt} = 0 \Rightarrow R \frac{dI}{dt} = -\frac{1}{C} I$$

$$\frac{dI}{I} = -\frac{dt}{RC} \quad \tau_c = RC$$

$$\frac{dI}{I} = -\frac{dt}{\tau_c} \Rightarrow \int_{i_0}^i \frac{dI}{I} = - \int_0^t \frac{dt}{\tau_c}$$

$$\ln \frac{i}{i_0} = -\frac{t}{\tau_c}$$

$$\frac{i(t)}{i_0} = e^{-t/\tau_c}$$

$$\Rightarrow i(t) = i_0 \cdot e^{-t/\tau_c}$$

$$i(t) = \frac{E}{R} \cdot e^{-t/RC}$$

